

Our math has to all be done with 1's and 0's. An Irish guy name Boole invented a way using logic.


e.g., Boolean Logic.

We'll use variables like  $x, y$  etc to represent inputs and outputs (of our logic circuits)  
Each variable can take on values of "1" or "0"

### Basic Operations

AND, OR, and NOT


Consider a switch (like a light switch)

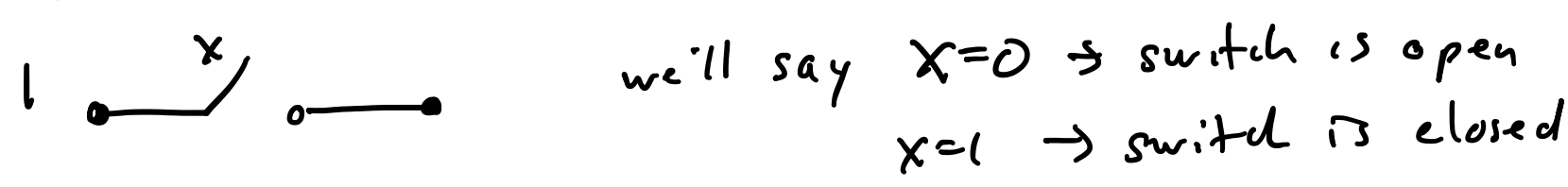

If switch is closed, the electricity get through to the light (not shown) and the light is on  
If switch is open, light is off

A switch can be "normally open" - think doorbell or normally closed (sensor on burglar alarm)

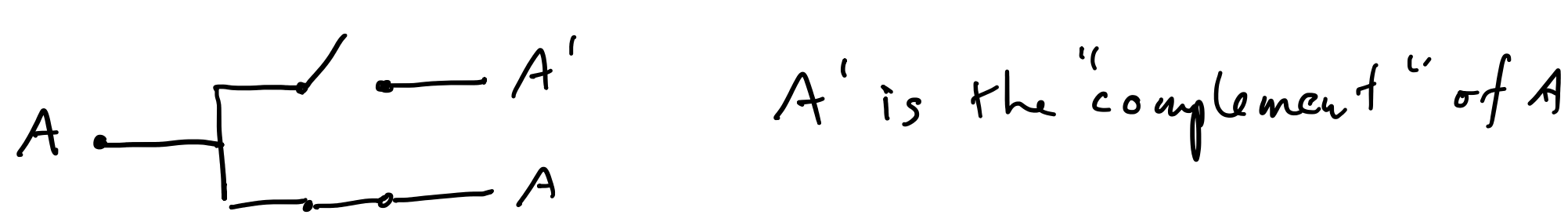Some switches are arranged with two outputs, such that if one is open the other is closed



or  $A' = \text{NOT } A$

We use a "NOT" gate or inverter  
"gate" is a circuit that does some logic


NOT gate:



Truth table


X	Y
0	1
1	0

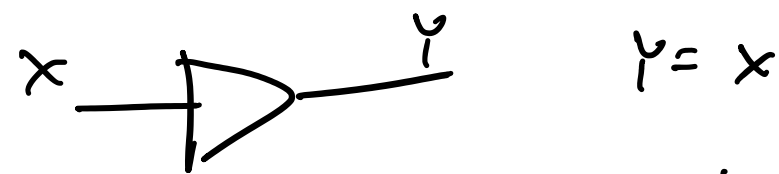Aside: this is the circuit symbol for a buffer



Doesn't perform any logic - used to amplify current or something.

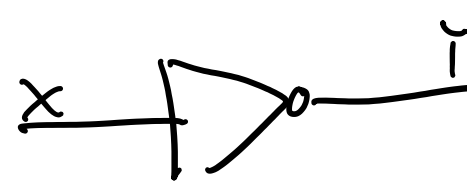But this is a NOT gate the bubble means "NOT"



That's the simplest logic gate.

Suppose you had  $x \xrightarrow{A} \text{switch} \xrightarrow{B} C$   
input is  $x \rightarrow$  let it be 1  
output is  $C$

There are four possible conditions:

- $A$  is open,  $B$  open
- $A$  open,  $B$  closed
- $A$  closed,  $B$  open
- $A$  closed,  $B$  closed

$A=0$  means switch is open


Truth Table

A	B	C
0	0	
0	1	
1	0	
1	1	

$\therefore C$  is only "true" (equal to 1) if both  $A$  and  $B$  are 1


$C = A \cdot B$   
"AND" - both have to be true to get a true output

Logic gate for that:

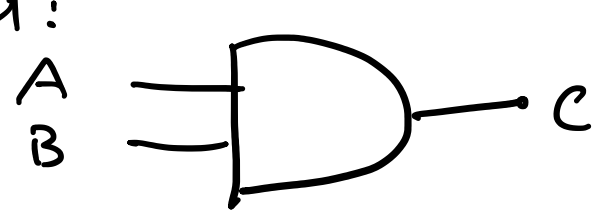

The dot means AND but we usually don't draw it

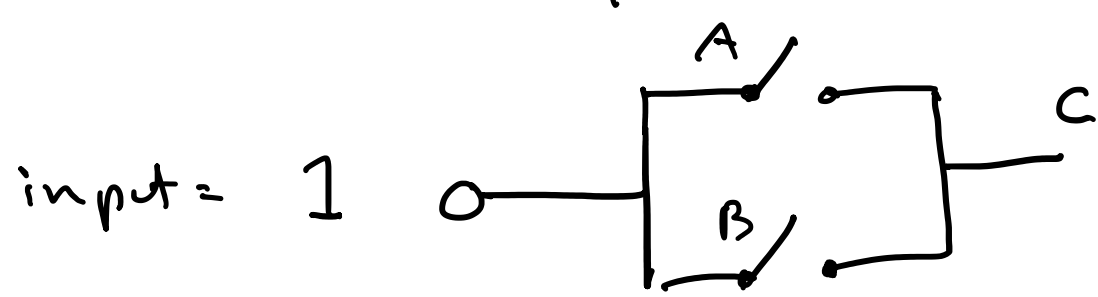Now, what if the switches are in parallel:



Now, if either switch is closed,  $C=1$

A	B	C
0	0	
0	1	
1	0	
1	1	

This function is called "OR"  
if A OR B is closed (or both) the output is 1

OR gate:



are "+" and "." the same as "add" or "multiply"?

OR

0	0	0	$0+0=0$ ✓
0	1		
1	0		
1	1		

AND

0	0	
0	1	
	0	
	1	

In lab, one of the early labs has you use a

"NOR" gate  $\rightarrow$  this is "NOT OR" or complement of "OR"

X	Y	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

What should the NOR gate look like?

Think OR + complement

There is also a NAND gate. NOT AND

X	Y	$X \text{ AND } Y$	NAND

These variables  $x, y, A, B, C$  etc are Boolean variables

NOT, OR, AND, etc are Boolean operators

We'll do more with them in the next section.